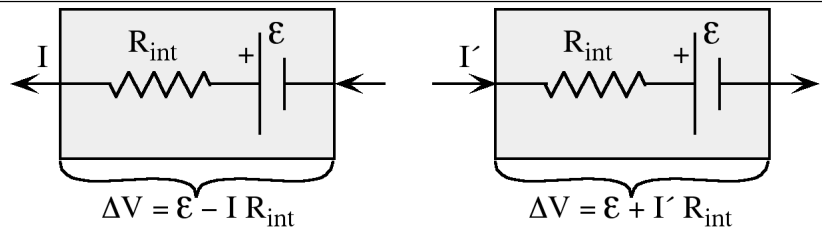


25 $J = E/\rho = (0.49\text{V/m})/(2.44 \times 10^{-8}\Omega \cdot \text{m}) = 2.0 \times 10^7 \text{A/m}^2$. Current = current/area \cdot area = $(2.0 \times 10^7 \text{A/m}^2)\pi(0.00042\text{m})^2 = 11.1\text{A}$. (b) $0.49\text{V/m} \cdot 6.4\text{m} = 3.14\text{V}$. (c) $R = \Delta V/I = (3.14\text{V})/11.1\text{A} = 0.283\Omega$

48 Suppose I guess I is clockwise. Starting from the negative of the 16V and going counterclockwise, I'll always be going across resistors *opposite* I, so V will increase. $+16 + I(1.6\Omega) + I(5\Omega) + I(1.4\Omega) - 8 + I(9\Omega) = 0$, or $8 + I(17\Omega) = 0$ or $I = -0.47\text{A}$. I conclude that the current is actually counterclockwise, at 0.47A. The power dissipated in the 5Ω is $I^2R = (0.47\text{A})(5\Omega) = 1.11\text{W}$. $P_{9\Omega} = (0.47\text{A})^2(9\Omega) = 1.99\text{W}$. Total: 3.1W. Current coming out of the 16V means it does work at the expense of its chemical energy, $P = IV = (0.47\text{A})(16\text{V}) = 7.53\text{W}$. Current going into the 8V means it stores energy, $P = IV = (0.47\text{A})(8\text{V}) = 3.76\text{W}$. Between the 16V and 8V "emf's", there is $7.53\text{W} - 3.76\text{W} = 3.76\text{W}$ of power delivered. 3.1W is burned up in the 5Ω and 9Ω, leaving 0.66W "unaccounted for". $P_{1.6\Omega} = I^2R = (0.47\text{A})^2(1.6\Omega) = 0.35\text{W}$. $P_{1.4\Omega} = (0.47\text{A})^2(1.4\Omega) = 0.31\text{W}$. Thus, these "internal resistances" are where the rest goes. So far as "power delivered by the 16V battery" goes, I guess you could say its $7.53\text{W} - 0.35\text{W} = 7.18\text{W}$, if we consider it as including its internal resistance, and the power "converted to other forms" in the 8V is $3.76\text{W} + 0.31\text{W} = 4.07\text{W}$, and the difference between these is the 3.1W burned up in the 5Ω and 9Ω.

60 This is resistors in series. $R = R_{Ag} + R_{Cu} = 1.47 \times 10^{-8}\Omega \cdot \text{m} \frac{1.2\text{m}}{\pi(0.0006\text{m}/2)^2} + 1.72 \times 10^{-8}\Omega \cdot \text{m} \frac{0.8\text{m}}{\pi(0.0006\text{m}/2)^2} = 0.0624\Omega + 0.0487\Omega = 0.111\Omega$. $I = V/R = 5\text{V}/0.111\Omega = 45\text{A}$. Both sections!
 (c) $E_{Cu} = j \rho_{Cu} = \frac{45\text{A}}{\pi(0.0006\text{m}/2)^2} 1.72 \times 10^{-8}\Omega \cdot \text{m} = 2.74\text{N/C}$. (d) $E_{Ag} = \frac{45\text{A}}{\pi(0.0006\text{m}/2)^2} 1.47 \times 10^{-8}\Omega \cdot \text{m} = 2.34\text{N/C}$
 (e) $\Delta V = IR = (45\text{A})(0.0624\Omega) = 2.81\text{V}$ or $\Delta V = E \Delta x = (2.34\text{V/m})(1.2\text{m}) = 2.81\text{V}$


69 While *delivering* power, from terminal to terminal ΔV is $\mathcal{E} - IR_{int}$. So $\mathcal{E} - (1.5\text{A})R_{int} = 8.4\text{V}$.
 When current goes the other way and it stores energy, the terminal to terminal potential difference is $\mathcal{E} + I'R_{int}$. So $\mathcal{E} + (3.5\text{A})R_{int} = 9.4\text{V}$



Solve the two equations in two unknowns however you like. $R_{int} = 0.2\Omega$ and $\mathcal{E} = 8.7\text{V}$

71 (a) $\rho_{\frac{L}{A}} = (5\Omega \cdot \text{m}) \frac{1.6\text{m}}{\pi(0.05\text{m})^2} = 1.02\text{k}\Omega$. (b) $IR = (0.1\text{A})(1.02 \times 10^3\Omega) \cong 100\text{V}$. Carpet variety shocks are kilovolts, but there is very little charge and the current lasts just an instant. (c) $I\Delta V = (0.1\text{A})(100\text{V}) = 10\text{W}$.

22 Looking at the top loop,
 $+20\text{V} - (1\text{A})(1\Omega) + I_3(4\Omega) + I_3(1\Omega) - \mathcal{E}_1 = 0$
 We could look at another loop now, but we'll save time by noting that by considering what goes on at either "node" *a* or *b*, where $I_1 + I_3 = I_2$, it must be that I_3 is 1A.
 $+20\text{V} - 1\text{V} + (1\text{A})(4\Omega) + (1\text{A})(1\Omega) - \mathcal{E}_1 - (1\text{A})(6\Omega) = 0$
 $\Rightarrow \mathcal{E}_1 = 18\text{V}$. Looking at the bottom loop and using $I_3 = 1\text{A}$,
 $\mathcal{E}_1 - (1\text{A})(1\Omega) - (1\text{A})(4\Omega) - (2\text{A})(1\Omega) - \mathcal{E}_2 - (2\text{A})(2\Omega) = 0$
 $\Rightarrow \mathcal{E}_2 = \mathcal{E}_1 - 11\text{V} = 7\text{V}$.
 From *a* to *b*, potential goes up by $(1\text{A})(4\Omega) + (1\text{A})(1\Omega) - 18\text{V} = -13$, so *b* is 13V lower in potential than *a*.

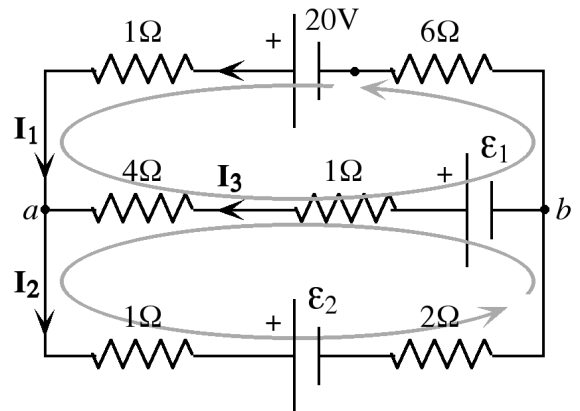

63 Right loop:

$$+36\text{V} - I_1 5\Omega - I_3 4\Omega = 0$$

Left loop:

$$+20\text{V} - I_2 2\Omega - 14\text{V} + I_3 4\Omega = 0 \text{ or } \mathbf{6\text{V} - I_2 2\Omega + I_3 4\Omega = 0}$$

$I_1 = I_2 + I_3$. The rest is math. Substituting for I_1 in the first,


$$+36\text{V} - (I_2 + I_3) 5\Omega - I_3 4\Omega = 0 \text{ or } \mathbf{36\text{V} - I_2 5\Omega - I_3 9\Omega = 0}.$$

Subtracting 5 times the first equation in bold from 2 times the second

$$\text{causes } I_2 \text{ to drop out: } 2 \cdot 36\text{V} - 2 \cdot I_3 9\Omega - 5 \cdot 6\text{V} - 5 \cdot I_3 4\Omega = 0.$$

$$\Rightarrow I_3 = 1.11\text{A. Plug back in: } 6\text{V} - I_2 2\Omega + (1.11\text{A}) 4\Omega = 0$$

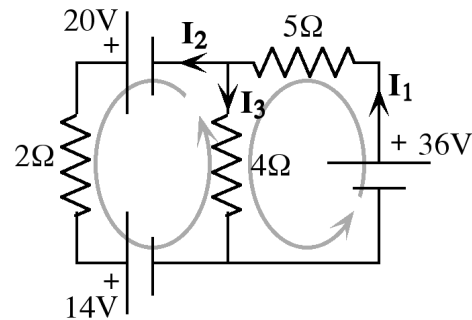$\Rightarrow I_2 = 5.21\text{A}$, and $I_1 = I_2 + I_3 = 6.32\text{A}$. All are positive, so we guessed direction correctly. In the right branch the current is 6.32A counterclockwise, in the center 1.11A downward, and in the left 5.21A counterclockwise.



74 (a&b) There will be twice the drop ($V_R = IR$) across the 6Ω as across the 3Ω , so the potential at a is 6V.

For the capacitors, on the other hand, $V_C = Q/C$. Assuming the switch was not previously closed (see end of problem), the capacitors are in series, with the same charge, so the smaller capacitance has the larger potential difference, again by a factor of 2. Thus, b is at 12V. (c) Once the switch is closed and the capacitors reach some final charged state, there will (again) just be a current through the resistors, so b , connected now to a by a perfect wire, will be at 6V. $Q_{6\mu\text{F}} = CV = (6 \times 10^{-6}\text{F})(12\text{V}) = 7.2 \times 10^{-5}\text{C}$, $Q_{3\mu\text{F}} = CV = (3 \times 10^{-6}\text{F})(6\text{V}) = 1.8 \times 10^{-5}\text{C}$. There is now a negative 7.2×10^{-5} on the lower plate of the $6\mu\text{F}$ and a positive 1.8×10^{-5} on the upper plate of the $3\mu\text{F}$, where before that conductor was (assumed) neutral. $5.4 \times 10^{-5}\text{C}$ of positive must have left this conductor through the switch. Because the capacitors' charges aren't equal now, opening the switch would not return everything to where it was at the beginning.

85 $Q = Q_0 e^{-t/RC} \rightarrow 1.6 \times 10^{-19}\text{C} = 7 \times 10^{-6}\text{C} e^{-t/(670 \times 10^3 \Omega \cdot 9.2 \times 10^{-7}\text{F})} \Rightarrow t = 19.4\text{s}$.

$RC = (670 \times 10^3 \Omega)(9.2 \times 10^{-7}\text{F}) = 0.616\text{s}$. $\frac{19.4}{0.616} = 31.4$. (b) A given Q_0 and a given Q_f , i.e., a single

elementary charge, means that $e^{-t/RC}$ is fixed, so t/RC is fixed, so t is a fixed multiple of RC . So it's always the same number of time constants, independent of what value the product RC might be. Of course, this does depend on the fact that Q_0 is fixed. A higher Q_0 would imply a longer wait till $Q_f = 1.6 \times 10^{-19}\text{C}$.

87 $\int \text{power} \cdot dt = \int_0^{\infty} \mathcal{E} \frac{\mathcal{E}}{R} e^{-t/RC} dt = \frac{\mathcal{E}^2}{R} (RC) = C \mathcal{E}^2$. (b) $\int \text{power} \cdot dt = \int_0^{\infty} \left(\frac{\mathcal{E}}{R} e^{-t/RC} \right)^2 R dt = \frac{\mathcal{E}^2}{R} (\frac{1}{2}RC) = \frac{1}{2} C \mathcal{E}^2$

(c) $U = \frac{1}{2} C \mathcal{E}^2$. Adds up. (d) Half. Doesn't depend on R . This is an irreversible process—you can't incrementally close a switch. And it will cause a certain entropy increase, whether it takes a long time (large R) or a short time (small R).